




Digital Integrated Circuits

A Design Perspective

Jan M. Rabaey
Anantha Chandrakasan
Borivoje Nikolic

Designing Sequential Logic Circuits


Sequential Logic

 



2 storage mechanisms

- positive feedback
- charge-based

Positive Feedback: Bi-Stability

 

Meta-Stability

  

Gain should be larger than 1 in the transition region



Naming Conventions

- In our text:
 - a latch is level sensitive
 - a register is edge-triggered
- There are many different naming conventions
 - For instance, many books call edge-triggered elements flip-flops
 - This leads to confusion however

Latch versus Register



❑ Latch

stores data when
clock is low

  


❑ Register

stores data when
clock rises

  


Latches

Positive Latch

 


Negative Latch

 



Latch-Based Design

- N latch is transparent when $\phi = 0$


- P latch is transparent when $\phi = 1$

 


Timing Definitions

  

Characterizing Timing

 


Register

 


Latch

Maximum Clock Frequency

 


Positive Feedback: Bi-Stability

 


Writing into a Static Latch

 Use the clock as a decoupling signal,
that distinguishes between the transparent and opaque states




Converting into a MUX

 

Forcing the state
(can implement as NMOS-only)


Mux-Based Latches

Negative latch
(transparent when CLK= 0)

 


$$Q = \overline{Clk} \cdot Q + Clk \cdot In$$

Positive latch
(transparent when CLK= 1)

 


$$Q = Clk \cdot Q + \overline{Clk} \cdot In$$


Mux-Based Latch

 

Mux-Based Latch (pseudo-static)

 


NMOS only

 

Non-overlapping clocks


Master-Slave (Edge-Triggered) Register

 


Two opposite latches trigger on edge
Also called master-slave latch pair

Master-Slave Register


Multiplexer-based latch pair

 


Reduced Clock Load Master-Slave Register

 

Avoiding Clock Overlap

 



(a) Schematic diagram

 

(b) Overlapping clock pairs

Overpowering the Feedback Loop — Cross-Coupled Pairs

NOR-based set-reset

 
 


S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
1	0	1	0
0	1	0	1
1	1	0	0

Forbidden State


Cross-Coupled NAND

Cross-coupled NANDs

  


This is not used in datapaths anymore,
but is a basic building memory cell

Sizing Issues

 


 Output voltage dependence
on transistor width




Transient response


Other Latches/Registers: C²MOS

 

Insensitive to Clock-Overlap

 


(a) (0-0) overlap

 


(b) (1-1) overlap

Other Latches/Registers: TSPC

 

Positive latch


(transparent when $CLK = 1$)

 


Negative latch

(transparent when $CLK = 0$)

Pipelining

 



Reference

 


Pipelined

Clock Period	Adder	Absolute Value	Logarithm
1	$a_1 + b_1$		
2	$a_2 + b_2$	$ a_1 + b_1 $	
3	$a_3 + b_3$	$ a_2 + b_2 $	$\log(a_1 + b_1)$
4	$a_4 + b_4$	$ a_3 + b_3 $	$\log(a_2 + b_2)$
5	$a_5 + b_5$	$ a_4 + b_4 $	$\log(a_3 + b_3)$


Latch-Based Pipeline

  

 
Non-Bistable Sequential Circuits— Schmitt Trigger



 
- VTC with hysteresis
- Restores signal slopes



Noise Suppression using Schmitt Trigger

 


CMOS Schmitt Trigger

 


**Moves switching threshold
of the first inverter**


Multivibrator Circuits

 

 Bistable Multivibrator
flip-flop, Schmitt Trigger




Monostable Multivibrator
one-shot

 


Astable Multivibrator
oscillator


Transition-Triggered Monostable

 

Monostable Trigger (RC-based)

 


(a) Trigger circuit.

 



(b) Waveforms.

Relaxation Oscillator

 



$$T = 2 (\log 3) RC$$

Astable Multivibrators (Oscillators)

  

simulated response of 5-stage oscillator

Voltage Controller Oscillator (VCO)

  

propagation delay as a function of control voltage